



Application Note: AN1200.54

SX1261 / SX1262 Adaptive Matching and Configuration for Multiband Operation

Table of Contents

1	Introduction	4
2	Transmitter Architecture	5
2.1	TxPower	6
2.2	PaDutyCycle	6
2.3	hpMax	6
3	Transmitter Configuration and Optimization	7
4	Receiver Architecture	14
5	Receiver Configuration and Optimization	15
6	Transmitter Adaptive Match Design Methodology	16
7	SX1261/2 Switchless Reference Design	17
7.1	SX1261/2 Switchless Reference Design schematic (E460V01A)	17
7.2	PCB Layout	19
7.3	BOM: 868 & 915 MHz Switchless RF Design	19
7.4	Adaptive Matching Configuration	20
8	SX1262 T/R Switch Reference Design	26
8.1	SX1262 T/R Switch Reference Design schematic (E428V03A)	26
8.2	PCB Layout	26
8.3	BOM: T/R Switch Reference Design	27
8.4	Adaptive Matching Configuration	27
8.5	Design Considerations	30
9	Receiver Adaptive Match Design Methodology	31
9.1	SX1261/2 Switchless Reference Design (E460V01A)	32
9.2	SX1262 T/R Switch Reference Design (E428V03A)	33
10	Conclusions	34
11	References	35
12	Revision History	36

List of Figures

Figure 1: Simplified Transmitter Architecture	5
Figure 2: Fundamental Tx Output Power as a Function of PaDutyCycle and hpMax	8
Figure 3: IDDTx as a Function of PaDutyCycle and hpMax	8
Figure 4: Second Harmonic Emissions as a Function of hpMax for PaDutyCycle = 2	9
Figure 5: Second Harmonic Emissions as a Function of hpMax for PaDutyCycle = 4	9
Figure 6: Third Harmonic Emissions as a Function of hpMax for PaDutyCycle = 2	10
Figure 7: Third Harmonic Emissions as a Function of hpMax for PaDutyCycle = 4	10
Figure 8: Second Harmonic Emissions as a Function of PaDutyCycle for hpMax = 4	11
Figure 9: Second Harmonic Emissions as a Function of PaDutyCycle for hpMax = 7	11
Figure 10: Third Harmonic Emissions as a Function of PaDutyCycle for hpMax = 4	12
Figure 11: Third Harmonic Emissions as a Function of PaDutyCycle for hpMax = 7	12
Figure 12: Simplified SX126x Receiver Front-End Architecture	14
Figure 13: SX1261/2 Switchless Reference Design Schematic - E460V01A	17
Figure 14: SX1262 Tx Zopt (+22 dBm)	18
Figure 15: SX126xMB1LDCS PCB Layout - E460V01A Top Layer RF Only	19
Figure 16: SX1262 Reference Design schematic - E428V03A	26
Figure 17: SX1262MB1CAS PCB Layout - E428V03A Top Layer RF Only	26

List of Tables

Table 1: TX and PA Configuration Variables	7
Table 2: SX1261/2 Switchless Reference Design (E460V01A) - BOM	19
Table 3: SX1262 Tx Characteristics as a Function of PaConfig (868.3 MHz; +14 dBm - Switchless)	21
Table 4: SX1262 Tx Characteristics as a Function of PaConfig (869.525 MHz; +22 dBm – Switchless)	22
Table 5: SX1262 Tx Characteristics as a Function of PaConfig (902.3 MHz; +22 dBm - Switchless)	22
Table 6: SX1262 Tx Characteristics as a Function of PaConfig (914.9 MHz; +22 dBm - Switchless)	22
Table 7: SX1262 Tx Characteristics as a Function of PaConfig (927.5 MHz; +22 dBm - Switchless)	23
Table 8: SX1262 Tx Characteristics as a Function of Tx and PaConfig (914.9 MHz; +14 dBm - Switchless)	23
Table 9: SX1261 Tx Characteristics as a Function of PaConfig (868.3 MHz; +14 dBm - Switchless)	24
Table 10: SX1261 Tx Characteristics as a Function of PaConfig (902.3 MHz; +14 dBm - Switchless)	24
Table 11: SX1261 Tx Characteristics as a Function of PaConfig (914.9 MHz; +14 dBm - Switchless)	25
Table 12: SX1261 Tx Characteristics as a Function of PaConfig (927.5 MHz; +14 dBm - Switchless)	25
Table 13: SX1262 T/R Switch Reference Design (E428V03A) - BOM	27
Table 14: SX1262 Tx Characteristics as a Function of PaConfig (868.3 MHz; +14 dBm - Switched)	27
Table 15: SX1262 Tx Characteristics as a Function of PaConfig (869.525 MHz; +22 dBm - Switched)	28
Table 16: SX1262 Tx Characteristics as a Function of PaConfig (869.525 MHz; +14 dBm - Switched)	28
Table 17: SX1262 Tx Characteristics as a Function of PaConfig (902.3 MHz; +22 dBm - Switched)	28
Table 18: SX1261 BOM changes for DC-DC mode configuration from SX1262MB1PAS Reference Design (E449V01A) - BOM	29
Table 19: SX1261 Tx Characteristics as a Function of PaConfig and Frequency (+14 dBm - Switched)	29
Table 20: 10% PER Threshold as a Function of Ina_cap_tune (Switchless Design)	32
Table 21: 10% PER Threshold as a Function of Ina_cap_tune (T/R Switch Design)	33

1 Introduction

Both the SX1261 and SX1262 low-power sub-GHz LoRa RF transceivers cover a wide frequency range, extending from 150 MHz up to 960 MHz.

Although the circuit itself covers this frequency range continuously, traditional circuit designs typically require several impedance-matching networks which, in turn, require multiple reference designs to meet both acceptable RF performance (in line with published specifications) and the specific requirements of various regulatory regimes to ensure compliance.

This Application Note describes a method in which the RF performance of a circuit can be configured by firmware to allow a single Bill Of Materials (BOM) to be implemented for both ITU Regions 1 and 2. This enables coverage over the frequency range 860 – 930 MHz, with particular reference to the **ETSI EN 300 220-1, CFR 47 Part 15 and ISSED / ISDE RSS-247 regulatory requirements**. This firmware configurability will demonstrate the flexibility of the SX1261 and SX1262 transmitter architecture.

It should be noted that the techniques described can be readily adapted for other frequency bands and regulatory domains.

The advantages of a firmware-configurable approach are:

- To provide a single design which may be adopted in multiple regions
- To enable an application to be used in multiple regions through a single hardware BOM
- Simplified logistical and support requirements

The Application Note further describes a switchless reference design, which takes advantage of the flexibility of the transceiver architecture to implement a reference design without the requirement for a switch between the antenna and the transmitter and receiver paths.

It is recommended to read this application note in conjunction with the following documents which can be found on www.semtech.com:

- SX1261/2 Datasheet
- Application Note AN1200.37: “Recommendations for Best Performance”
- Application Note AN1200.40: “Reference Design Explanation for the SX1261/62”
- Application Note AN1200.79: “SX1261 and SX1262 Switchless Design Description and Prescan Report”

2 Transmitter Architecture

A simplified block diagram of the power amplifier (PA) architecture is illustrated in Figure 1.

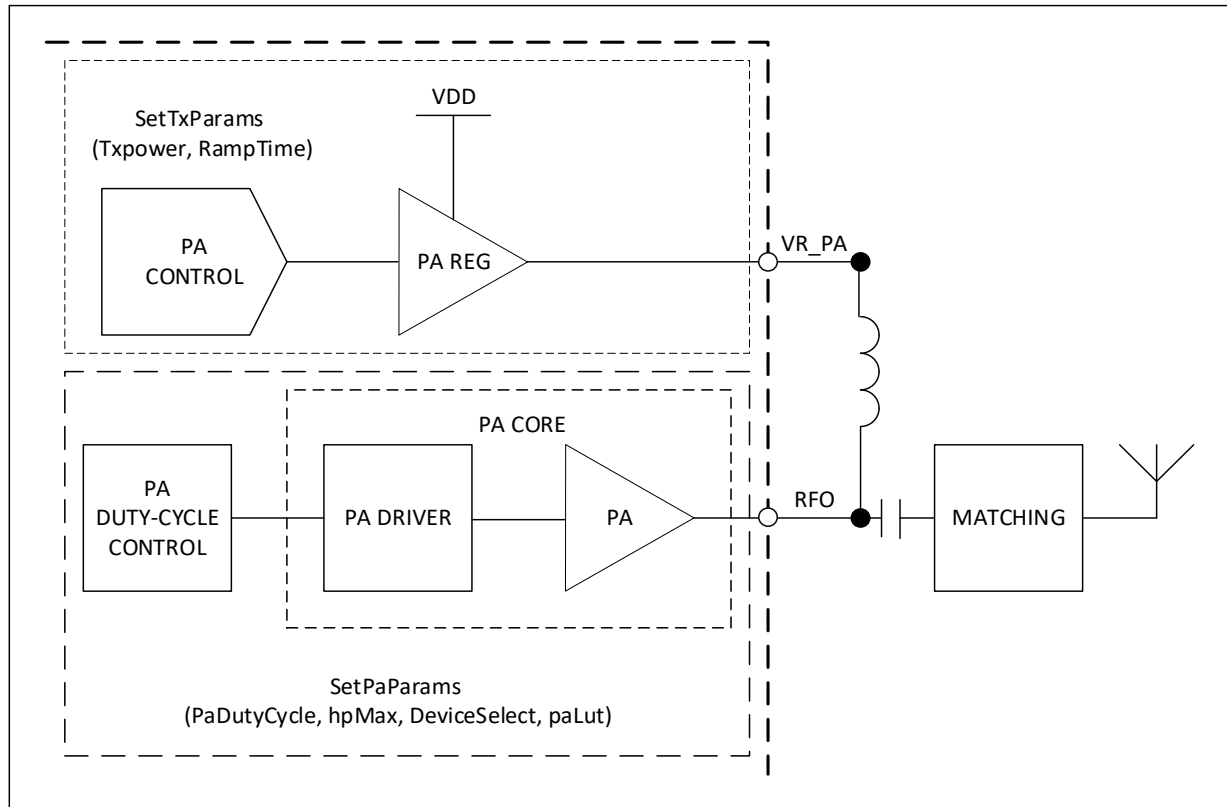


Figure 1: Simplified Transmitter Architecture

The PA architecture of the SX1261 and SX1262 is flexible by design, and capable of delivering a wide output power range without sacrificing efficiency. This architecture, shown above, uses three configurable parameters to control the output power, **TxPower**, **PaDutyCycle** and **hpMax**.

Both the output power and current consumption increase with an increase in any one of the above parameters. However, the behaviour of the overall efficiency and the harmonic levels vary differently depending on which parameter is used to control functionality, as described in the following sections.

2.1 TxPower

Configuration of the **TxPower** parameter sets the voltage supply of the PA (VR_PA). For the purposes of the examples considered by this application note, **TxPower** is configured to a maximum, which sets VR_PA to a maximum and maximizes the efficiency of the circuit. However, as is also demonstrated, the configured **TxPower** can be adapted to provide for a degree of fine-tuning, as required. Further information relating to configured output power as a function of VR_PA can be found in Section 4.4 of the SX1261/2 datasheet [\[1\]](#).

2.2 PaDutyCycle

The **PaDutyCycle** parameter controls the duty cycle of the PA driver stage, which is equivalent to controlling the conduction angle of a class C amplifier. It will be demonstrated that both output power and current consumption increase with higher duty cycles. Therefore, it is recommended that the **PaDutyCycle** should be kept as low as possible to maximize efficiency. Note that the relative amplitude of odd and even harmonics are a function **PaDutyCycle**.

The valid range of **PaDutyCycle** for SX1262 is 0 to 4 (for **hpMax** 0 to 7) or 0 to 7 for (**hpMax** = 0 to 4) and 0 to 7 for SX1261 for synthesized frequencies greater than 400 MHz.

2.3 hpMax

The third parameter, **hpMax**, configures the number of stages in the high-power amplifier (HPA) block. As the number of stages increase so do the output power and current consumption. In addition, it should be noted that harmonic emissions similarly increase with increasing output power. For maximum efficiency, **hpMax** should be configured to the lowest possible value required to achieve the desired output power. Note that the balance of configured **PaDutyCycle** and **hpMax** parameters will be both circuit and application dependent.

The valid range of **hpMax** is 0 to 7. Above this upper limit, degradation to the SX1262 PA structure may occur. Note the SX1261 low-power amplifier LPA block is similar to that of the HPA stage of the SX1262. However, there is no additional configuration of this stage and **hpMax** should be set to "0" for the SX1261.

3 Transmitter Configuration and Optimization

Sections 11.1 and 13.1.14 of the SX126x datasheet describe the optimal configuration of the PaConfig parameters for given "narrow-band" or region-specific cases.

The configuration of the transmitter architecture is defined by the following:

- Radio.SetTxParams (**TxPower**, RampTime)
- Radio.Set PaConfig (**PaDutyCycle**, **hpMax**, DeviceSelect, paLut)

As described in Section 2, the transceiver is configured for maximum output power to maximize both VR_PA and efficiency. RampTime is selected to ensure any transient or switching spectrum complies with regulatory requirements.

The recommended range of both TxParams and PaConfig variables for operation over the frequency range 863 – 928 MHz is tabulated below in Table 1.

Parameter	Range	
	SX1261	SX1262
TxPower (dBm)	-17 to +14	-9 to +22
RampTime (μs)	10 to 3400	
PaDutyCycle	0 to 7	0 to 4
hpMax	1	0 to 7
DeviceSelect	1	0
paLut	1	

Table 1: TX and PA Configuration Variables

To observe the effect on the emissions spectrum and current consumption, as a function of the configuration of both **hpMax** and **PaDutyCycle** parameters, a representative SX1262 switched reference design, version E428V03A and as illustrated in Figure 16, is configured to operate over the frequency range from 860 MHz to 935 MHz, with **TxPower** configured to +22 dBm.

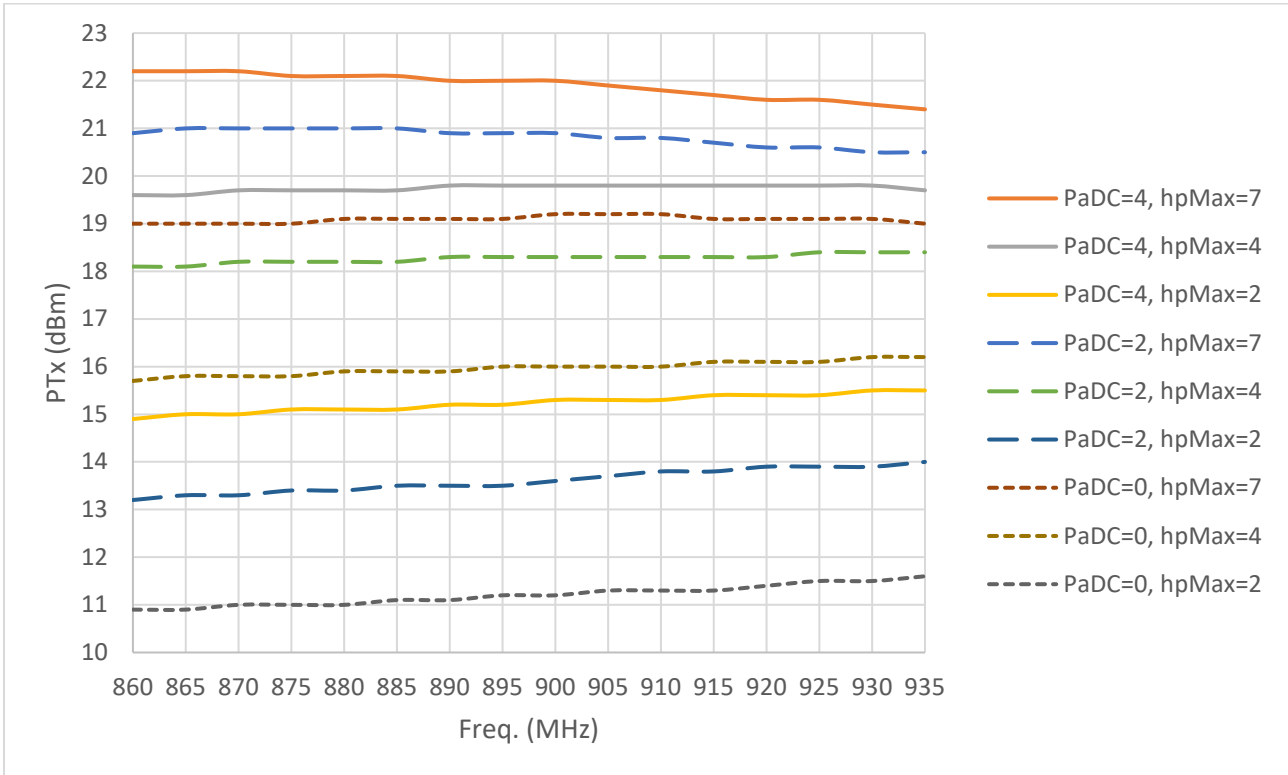


Figure 2: Fundamental Tx Output Power as a Function of PaDutyCycle and hpMax

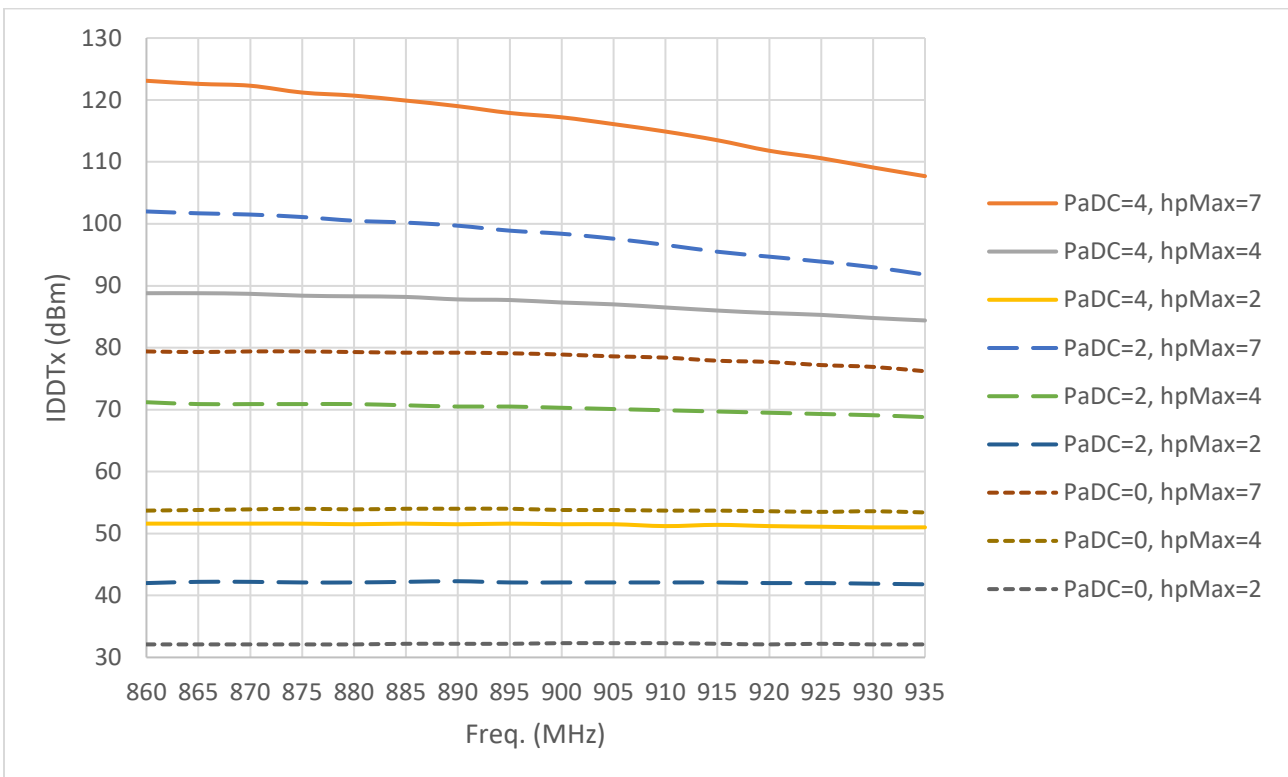


Figure 3: IDDTx as a Function of PaDutyCycle and hpMax

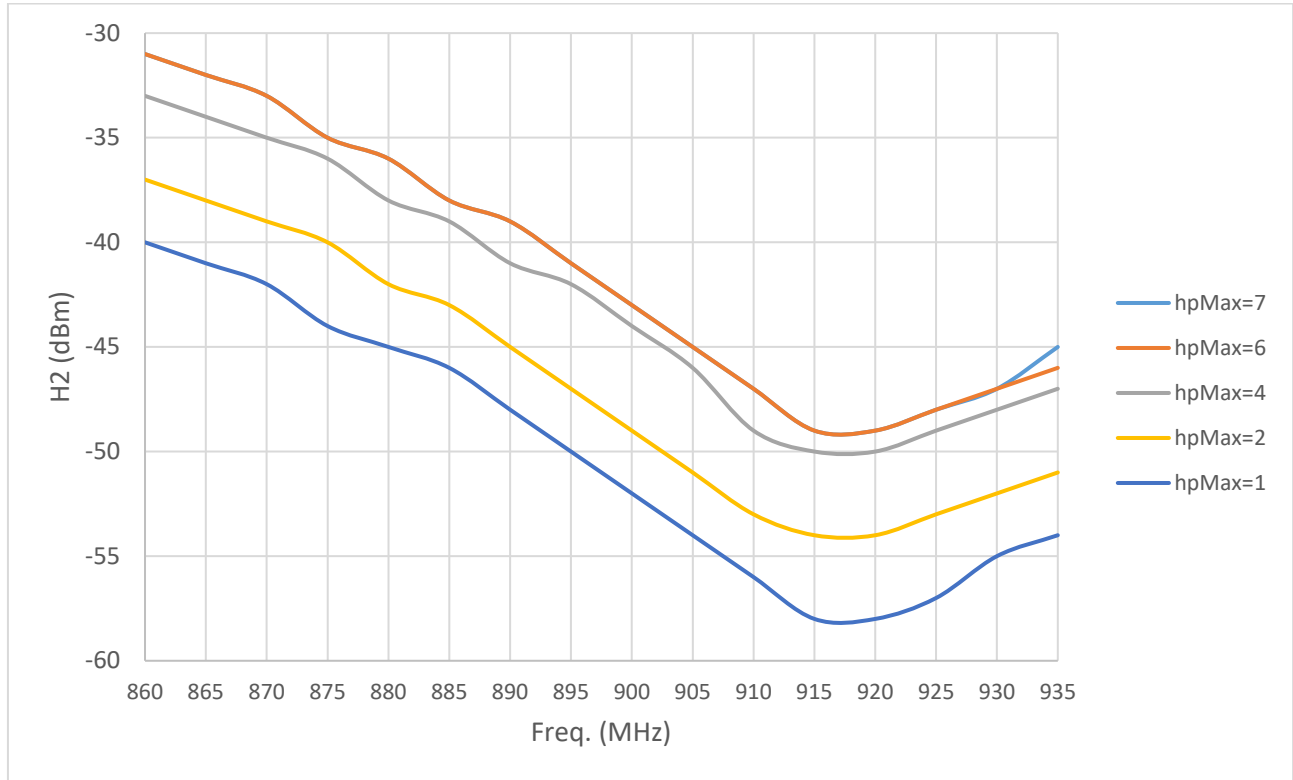


Figure 4: Second Harmonic Emissions as a Function of hpMax for PaDutyCycle = 2

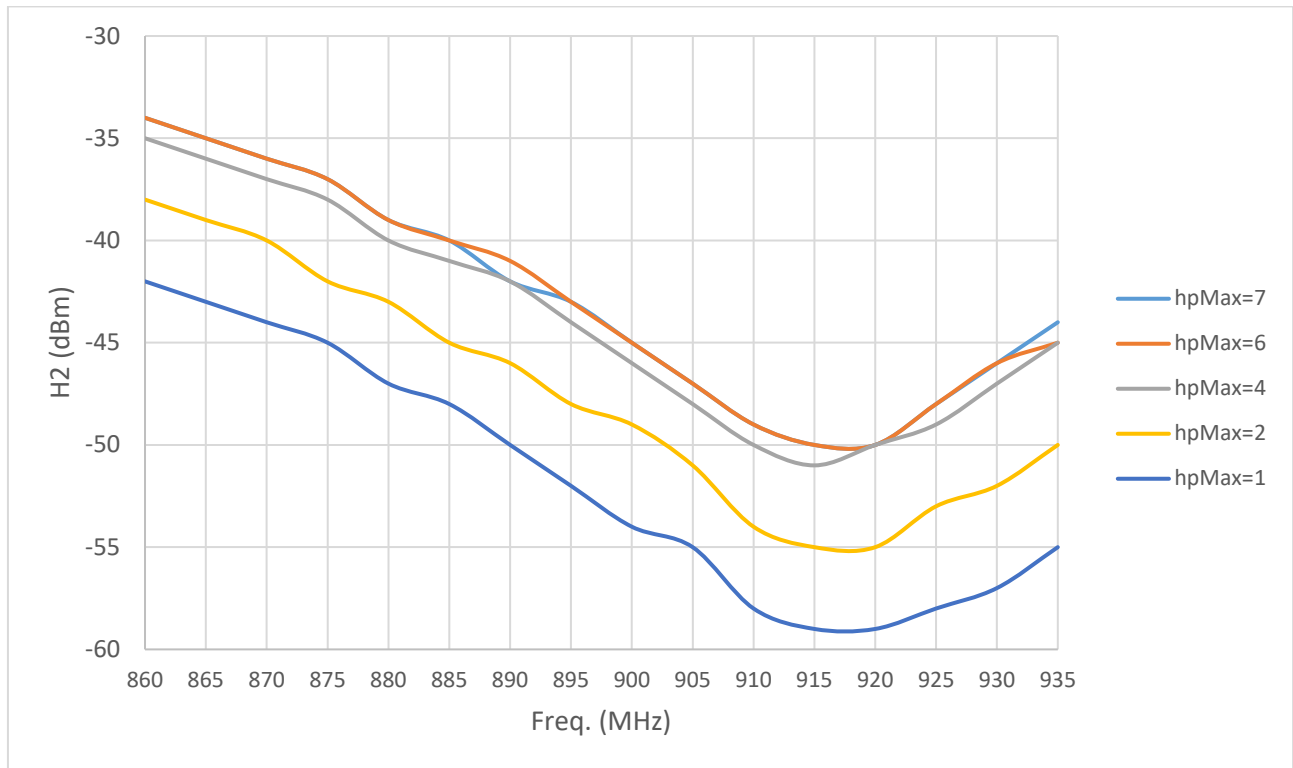


Figure 5: Second Harmonic Emissions as a Function of hpMax for PaDutyCycle = 4

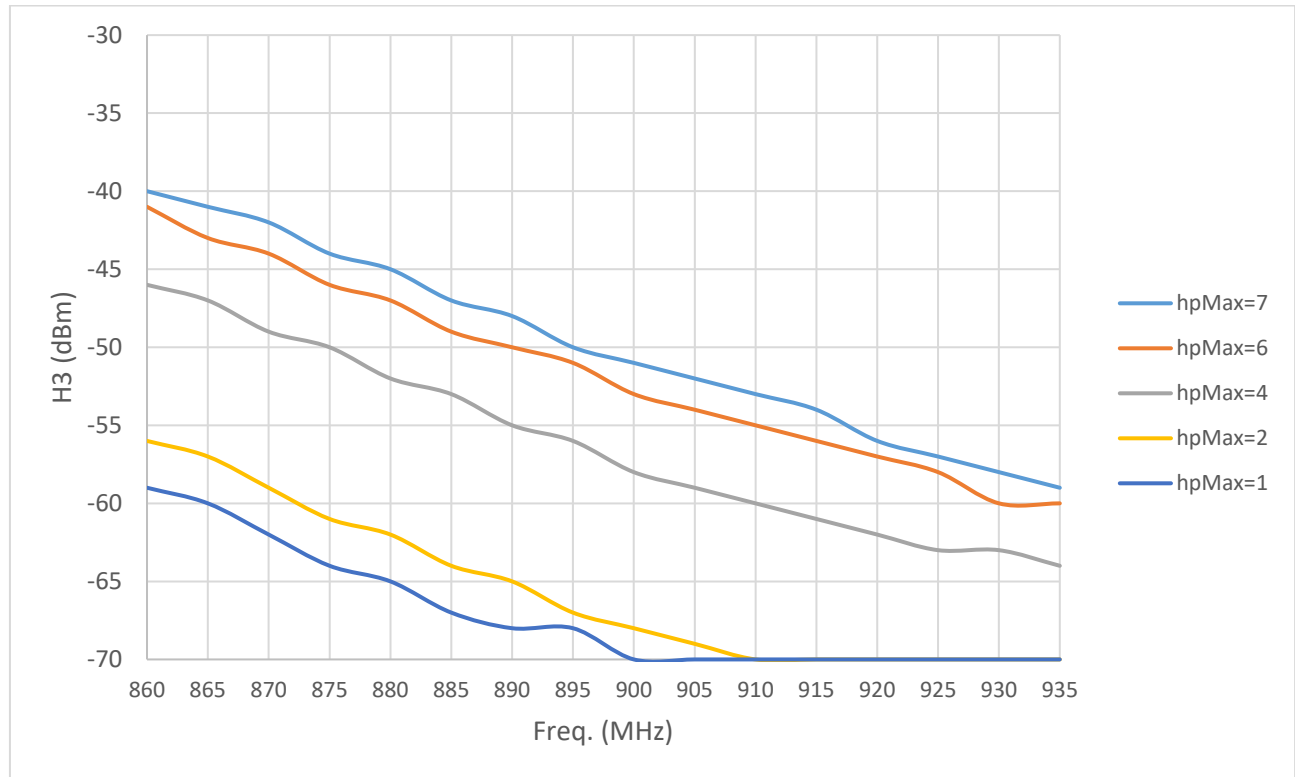


Figure 6: Third Harmonic Emissions as a Function of hpMax for PaDutyCycle = 2

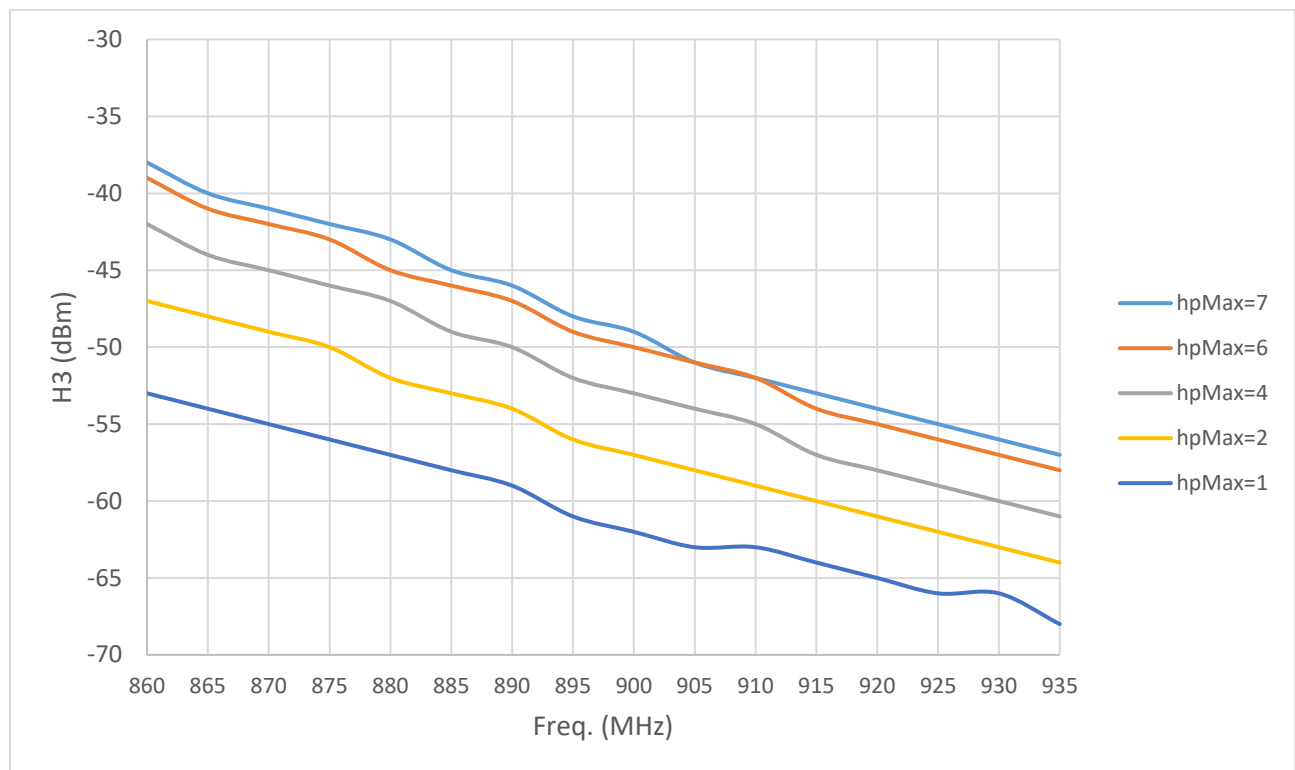


Figure 7: Third Harmonic Emissions as a Function of hpMax for PaDutyCycle = 4

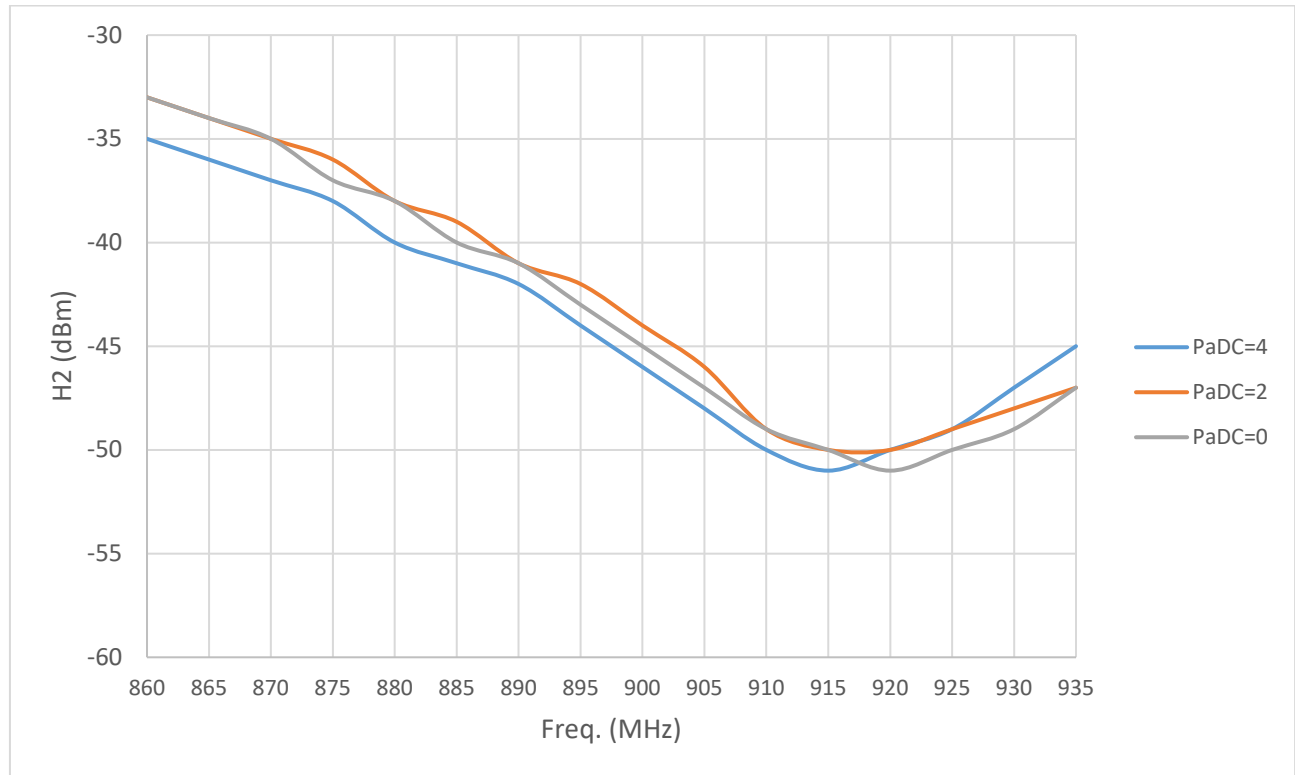


Figure 8: Second Harmonic Emissions as a Function of PaDutyCycle for hpMax = 4

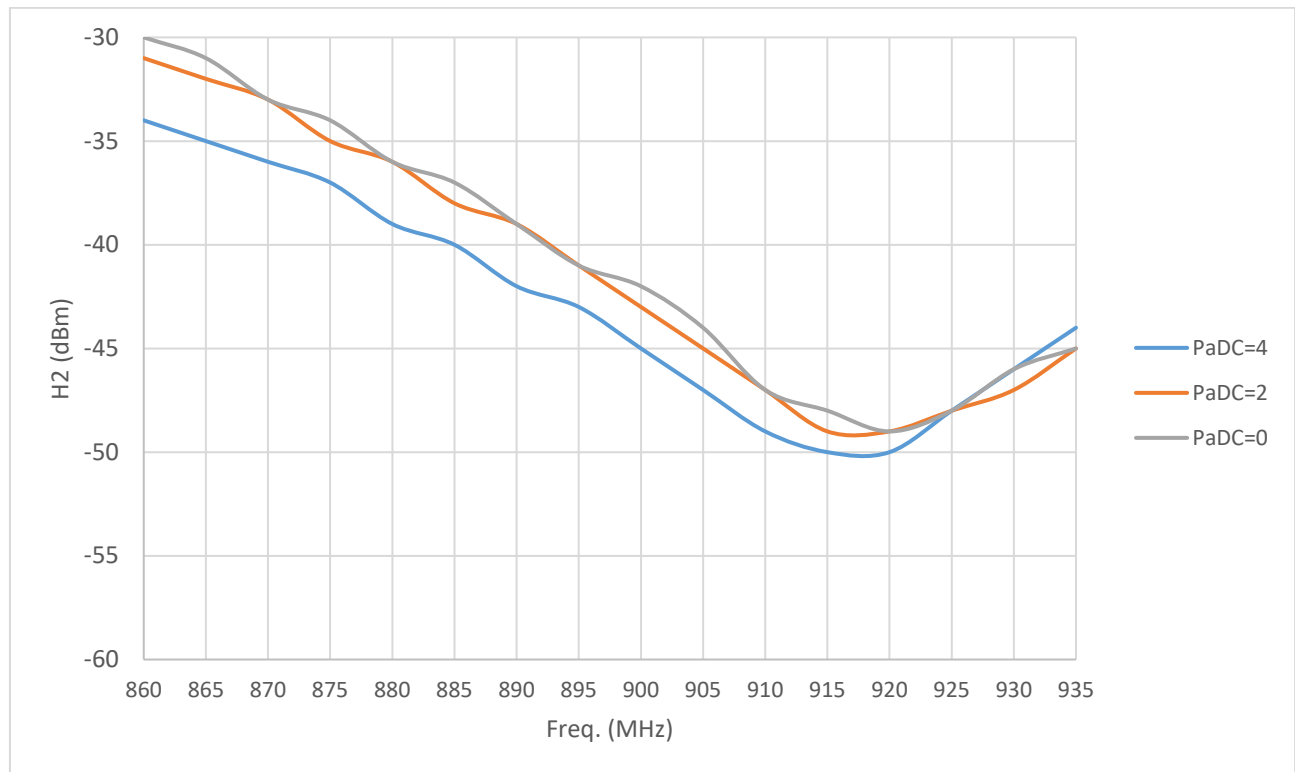


Figure 9: Second Harmonic Emissions as a Function of PaDutyCycle for hpMax = 7

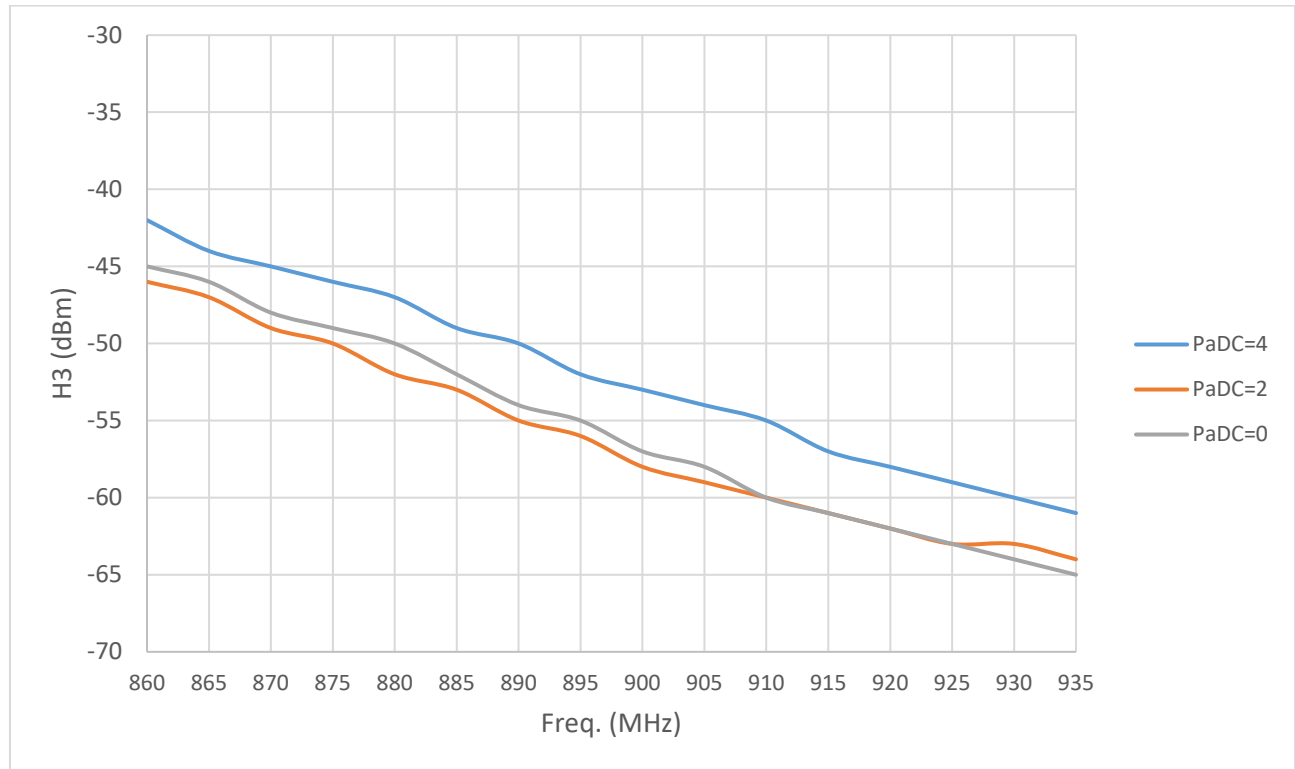


Figure 10: Third Harmonic Emissions as a Function of PaDutyCycle for hpMax = 4

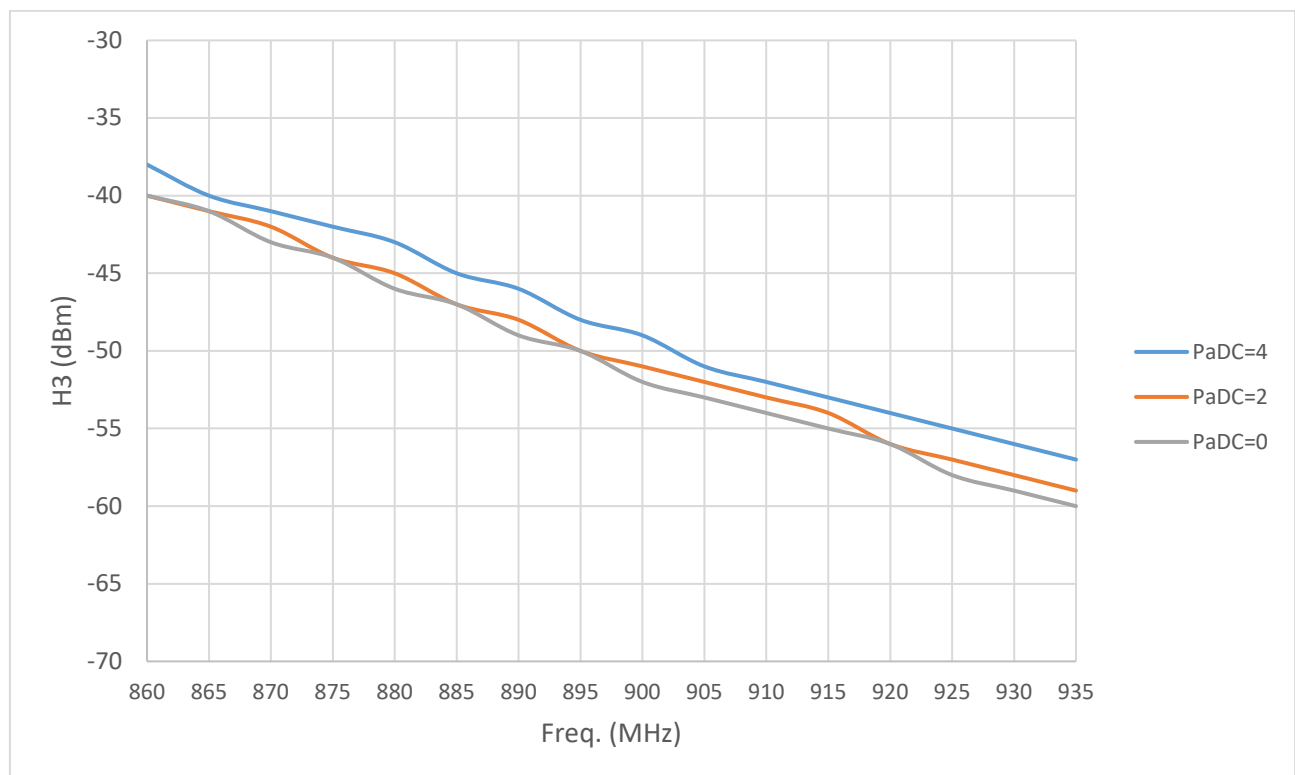


Figure 11: Third Harmonic Emissions as a Function of PaDutyCycle for hpMax = 7

From the results illustrated above, it can be observed that for a fixed **TXPower**, configuration of both **PaDutyCycle** and **hpMax** parameters can be used to modify the emissions signature and as will be demonstrated, the efficiency of both SX1261 and SX1262.

Maximum indicated fundamental output power, P_{Tx} , is obtained for the maximum configured values of **PaDutyCycle** and **hpMax**. In general, increasing **hpMax** increases the output power and all harmonics. On the other hand, the behaviour of the individual harmonic components is a function of **PaDutyCycle** configured.

Note that for the case where **PaDutyCycle** is set to zero, this specific configuration will result in the lowest transmitter output power and transmit mode current consumption. However, it does not result in maximum efficiency and relative to the fundamental wanted emission, will lead to the highest relative harmonic emission levels.

It should also be noted that the load impedance presented by the matching network at the RFO port and the characteristics of the matching network will also exert an influence upon the measured parameters.

As this Application Note will show, through a combination of hardware BOM and firmware configuration both SX1261 and SX1262 can adapted to meet both regulatory and application requirements over a wide frequency range that encompasses both the European and America regions.

4 Receiver Architecture

A simplified block diagram of the differential receiver architecture is illustrated in Figure 12.

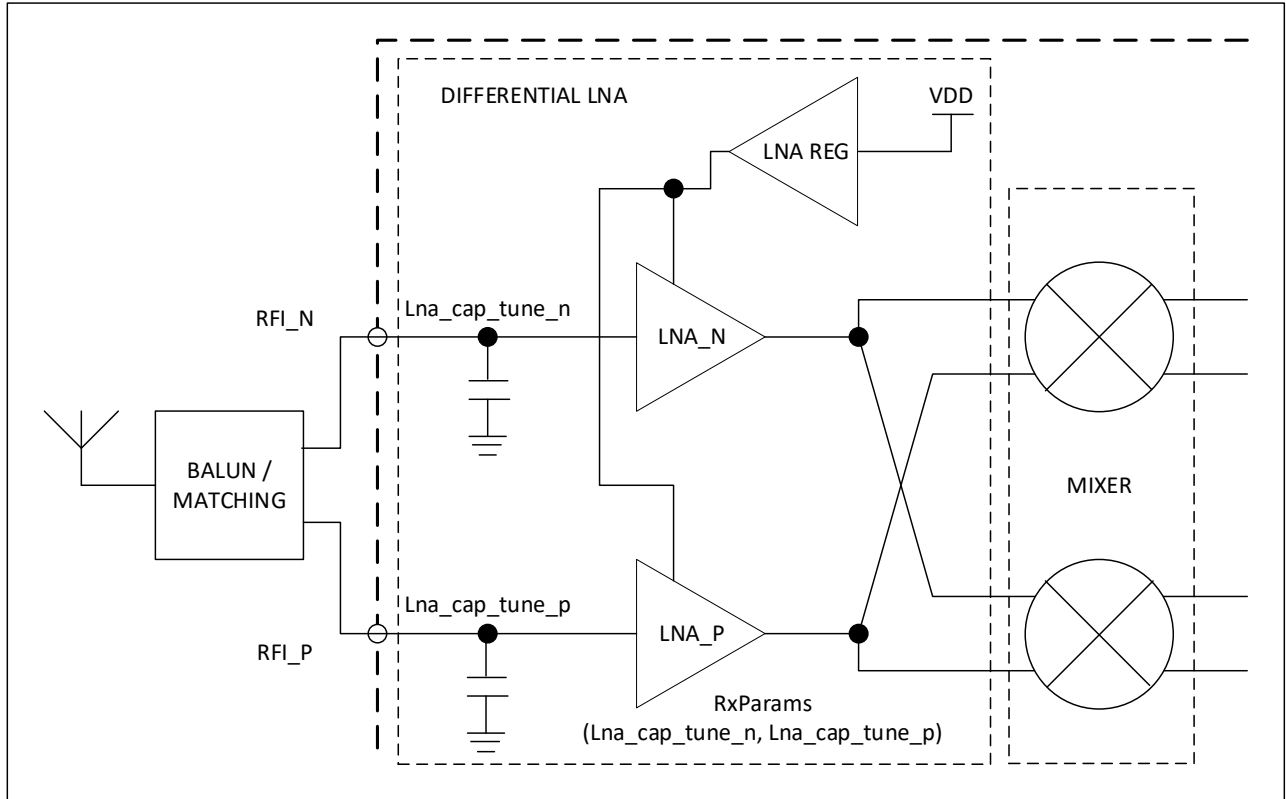


Figure 12: Simplified SX126x Receiver Front-End Architecture

The balun and matching circuit of the SX1261 and SX1262 reference designs provides for a broadband optimum match between the differential input structure of LNA and the single-ended nominal 50 ohm impedance of either the RF switch or antenna feed-point. However, for some applications the topology and routing of this network may require additional matching network optimization.

As an alternative to hardware optimization, it is possible to "tune" the input impedance of the LNA and thus the effective capacitive loading at the ports, through independently configuring the input shunt capacitances. These are identified in the figure above as **lna_cap_tune_n** (accessible at bits [3:0] at address 0x08E3) and **lna_cap_tune_p** (accessible at bits [7:4] at address 0x08E4) and both can be varied over a typical 0.8pF range in increments of 50fF per LSB.

The default value of **lna_cap_tune** is 0100b, equivalent to an additional 0.2 pF loading across each port.

5 Receiver Configuration and Optimization

Section 9.6 of the SX1261/2 datasheet describes the optimal configuration of the receiver parameters. As documented in Section 4 of this Application Note, the input capacitive loading of the differential LNA inputs can be configured to accommodate either a non-optimal implementation of the receiver matching network or where modification to the BOM may influence the performance of the transmitter circuit.

To observe the effects of changing the configuration of the capacitive loading at each port a simple packet error rate (PER) measurement is performed at the frequencies of interest for each possible configuration of **lna_cap_tune_n** and **lna_cap_tune_p** in turn.

This process will reveal a range of values of **lna_cap_tune_n** and **lna_cap_tune_p** over which an optimized sensitivity level is indicated, subject to the granularity provided by the PER measurement. It is recommended that the identified range be verified on several devices to ensure the component tolerances of the external matching network are taken into consideration.

6 Transmitter Adaptive Match Design Methodology

In this section, a method illustrating how both the PA configuration and hardware matching networks can be optimized to provide a broadband response capable of satisfying the relevant regulatory requirements of both European and North American regulations over a frequency range from 863 - 928 MHz with a single hardware BOM.

Again, this will be achieved by simply reconfiguring the on-chip amplifier stage to compensate for variation in the characteristics presented to the TX port by the RF matching network over the frequency range of interest, using the methodology described in Section 3.

This approach can also be used to assist in compensating for the characteristics of a particular matching network or layout topology. However, it is not a substitute for good RF design practices.

Semtech has developed the adaptive match reference design for SX1261/2 version E460V01A, which does not require a T/R switch. However, this Application Note will also consider the further analysis of the switched design introduced in Section 3.

Note that for the description of the adaptive match design methodology, the Application Note defines two additional parameters, η_{SX} , the efficiency of the entire radio circuit and η_{PA} , the efficiency of the PA circuit. These additional parameters may be considered when deciding upon the optimum configuration for power-constrained or battery-operated applications.

$$\eta_{SX} = \left(\frac{RF \text{ Output Power}}{DC \text{ Input Power}} \right) * 100\% = \left(\frac{10^{\left(\frac{PTX(dBm)}{10}\right)}}{VDD_RADIO * IDDTX} \right) * 100\%$$

$$\eta_{PA} = \left(\frac{RF \text{ Output Power}}{PA \text{ DC Power}} \right) * 100\% = \left(\frac{10^{\left(\frac{PTX(dBm)}{10}\right)}}{VR_PA * IDDTX} \right) * 100\%$$

7 SX1261/2 Switchless Reference Design

7.1 SX1261/2 Switchless Reference Design schematic (E460V01A)

In the following example, we consider the 868 MHz and 915 MHz SX126xMB1LDCS mbed shield reference design PCB_460V01A illustrated in Figure 13, to demonstrate the versatility of the adaptive match PaConfig parameter configuration approach. This shield is only available as a published reference design [2].

The schematic of the switchless reference design is illustrated in Figure 13.

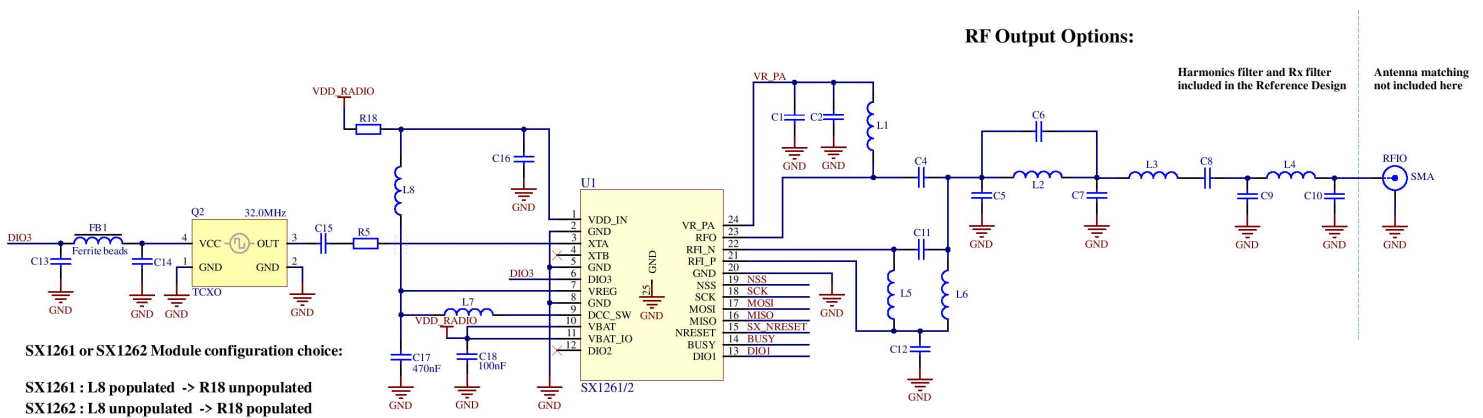


Figure 13: SX1261/2 Switchless Reference Design Schematic - E460V01A

From the schematic diagram, it can be observed that the receiver (RFI) and transmitter (RFO) ports are connected at the junction of C4, C11, C5.

The receiver matching network is a classic lumped-element balun formed by C11, C12, L6 (L5 is not populated), while for the transmitter circuit, the matching network is a cascaded low-pass filter topology with the addition of a harmonic trap formed by C6 in parallel with L2.

To match the TX, a cascaded low-pass filter stage is developed from the nominal 50 Ohm port of the antenna back to the optimum load impedance (Z_{opt} or S_{22}^*) of the RFO port for +22 dBm operation at the frequencies of interest. As illustrated in Figure 14, the optimum load impedance at both 868 MHz and 915 MHz are similar and either point may be selected.

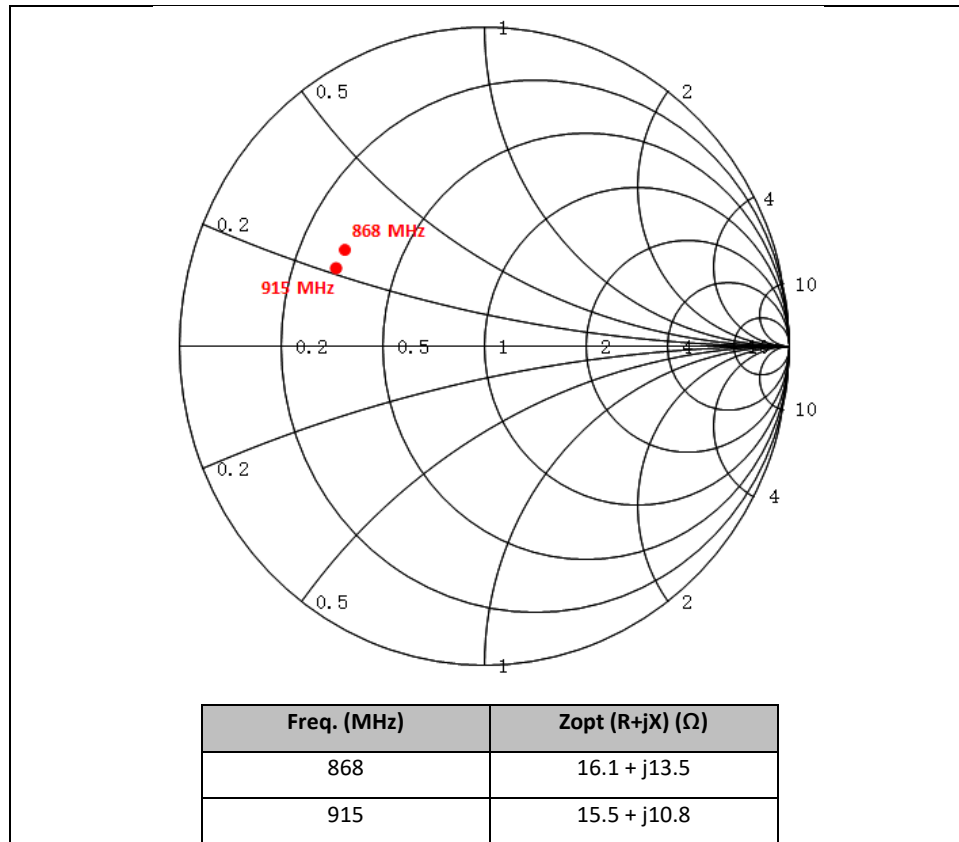


Figure 14: SX1262 Tx Zopt (+22 dBm)

With the receiver network isolated from the transmitter, the low-pass matching network is developed. During this process, C6 is not populated and a value of L2 in the range 3.0 nH – 3.3 nH is selected. With the match optimized, L2 is set in the range typically 0.75 – 0.8 of that initially selected above, and C6 is selected to ensure good rejection of H2 in the 863 – 870 MHz band, while not significantly degrading the H3 response when operating in the 902 – 928 MHz band.

Finally, we populate the receiver matching network. The component values of the BOM should be used.

Since this matching network will “pull” the matching network impedance presented to the transmitter circuit, fine-tuning of the transmitter matching network may be required.

7.2 PCB Layout

The SX1261/2 switchless E460V01A mbed shield is designed on a low-cost standard 4-layer FR-4 substrate. The top layer houses all the components and critical RF layout. Layer 2 serves as the reference ground for all RF circuits. Layer 3 is used for control routing, and layer 4 is solid ground.

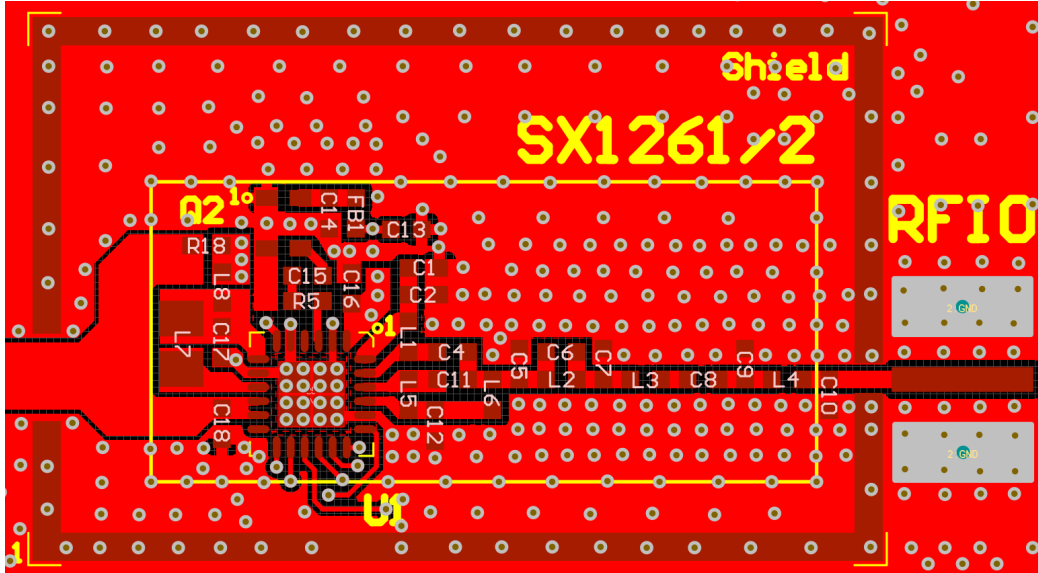


Figure 15: SX126xMB1LDCS PCB Layout - E460V01A Top Layer RF Only

7.3 BOM: 868 & 915 MHz Switchless RF Design

The BOM for the TX and RX matching networks is as documented below:

RefDes	Package	Value	Qty	Description	Manufacturer
C1	0402	47nF	1	Multilayer ceramic capacitors X7R $\pm 10\%$, 16V	Murata
C2	0402	47pF	1	Multilayer ceramic capacitors C0G $\pm 5\%$, 50V	Murata
C4	0402	47pF	1	Multilayer ceramic capacitors C0G $\pm 5\%$, 50V	Murata
C5	0402	NC	0	Not Populated	Murata
C6	0402	3.0pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C7	0402	5.6pF	1	Multilayer ceramic capacitors C0G $\pm 0.25\text{pF}$, 50V	Murata
C8	0402	47pF	1	Multilayer ceramic capacitors C0G $\pm 5\%$, 50V	Murata
C9	0402	5.6pF	1	Multilayer ceramic capacitors C0G $\pm 0.25\text{pF}$, 50V	Murata
C10	0402	3.3pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C11	0402	4.0pF	1	Multilayer ceramic capacitors C0G $\pm 0.25\text{pF}$, 50V	Murata
C12	0402	3.9pF	1	Multilayer ceramic capacitors C0G $\pm 0.25\text{pF}$, 50V	Murata
L1	0402	47nH	1	Wirewound Inductor $\pm 5\%$	Murata
L2	0402	2.7nH	1	Wirewound Inductor $\pm 0.2\text{nH}$	Murata
L3	0402	2.7nH	1	Wirewound Inductor $\pm 0.2\text{nH}$	Murata
L4	0402	8.2nH	1	Wirewound Inductor $\pm 3\%$	Murata
L5	0402	10nH	1	Wirewound Inductor $\pm 3\%$	Murata
L6	0402	NC	0	Not Populated	Murata

Table 2: SX1261/2 Switchless Reference Design (E460V01A) - BOM

7.4 Adaptive Matching Configuration

Adaptive matching configuration of the PA is then implemented to fine-tune the response of the SX1262 to meet the requirements for the specific application.

As an example, the application scenarios described below are considered:

1. Operation as a default LoRaWAN channel operating in Band h1.4 of Annex 1 of ERC 70-03 [\[4\]](#) at 868.3 MHz with an approximate ERP of 25 mW (+14 dBm).
2. Operation as a LoRaWAN channel operating in Band h1.7 of Annex 1 of ERC 70-03 at 869.525 MHz with an approximate ERP of 158 mW (+22 dBm).
3. Operation as a LoRaWAN channel operating under the auspicious of CFR 47 Part 15.247 with an approximate output power of +22 dBm.

First, consider the case for operating at 868.3 MHz with a nominal output power of +14 dBm as documented below in Table 3.

Introducing PaConfig parameter annotation (m; n) to denote the configuration setting for **PaDutyCycle** and **hpMax** values respectively, the results indicate that PaConfig parameters (0; 3), (2; 2), (3; 2) (4; 2) set a fundamental output power of approximately +14 dBm. Configuration PaConfig(2; 2) provides for the lowest current consumption and good harmonic balance, while configuration PaConfig(3; 2) indicates the conditions for maximum efficiency.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)						η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6		
0	1	19.5	3.10	5.7	-44	≤ -70	≤ -70	≤ -70	≤ -70	6.13	5.76
0	2	31.8	3.11	11.0	-43	≤ -70	≤ -70	≤ -70	≤ -70	12.73	12.00
0	3	43.4	3.12	14.0	-42	≤ -70	≤ -70	≤ -70	≤ -70	18.38	17.38
0	7	75.5	3.14	18.7	-39	-61	≤ -70	≤ -70	-66	31.27	29.75
...
1	1	22.2	3.10	7.2	-45	≤ -70	≤ -70	≤ -70	≤ -70	7.57	7.11
1	2	36.9	3.11	12.4	-43	≤ -70	≤ -70	≤ -70	≤ -70	15.14	14.27
1	3	50.3	3.12	15.3	-42	-67	≤ -70	≤ -70	≤ -70	21.59	20.41
1	4	61.5	3.13	17.1	-41	-63	≤ -70	≤ -70	-66	26.64	25.27
...
1	7	85.0	3.14	19.6	-40	-60	≤ -70	≤ -70	-66	34.17	32.51

2	1	24.9	3.10	8.3	-46	≤ -70	≤ -70	≤ -70	≤ -70	8.76	8.23
2	2	41.8	3.12	13.5	-44	-67	≤ -70	≤ -70	≤ -70	17.17	16.23
2	3	57.3	3.13	16.3	-43	-64	≤ -70	≤ -70	≤ -70	23.78	22.56
...
2	7	95.5	3.14	20.4	-42	-57	≤ -70	≤ -70	-66	36.57	34.79

3	1	46.8	3.12	14.3	-46	-66	≤ -70	≤ -70	≤ -70	9.79	9.20
3	2	46.8	3.12	14.3	-46	-66	≤ -70	≤ -70	≤ -70	18.43	17.43
...
3	7	107.9	3.16	21.2	-47	-56	≤ -70	≤ -70	-65	38.66	37.02

4	1	32.0	3.11	9.9	-48	-68	≤ -70	≤ -70	≤ -70	9.86	9.30
4	2	54.1	3.12	14.9	-49	-62	≤ -70	≤ -70	≤ -70	18.31	17.31
...
4	7	123.4	3.17	21.8	-56	-55	≤ -70	≤ -70	-62	38.51	37.00

Table 3: SX1262 Tx Characteristics as a Function of PaConfig (868.3 MHz; +14 dBm - Switchless)

In the second application scenario, operating at 869.525 MHz with a nominal output power of +22 dBm is required and the same process can be repeated, as shown in Table 4.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)						η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6		
3	7	107.8	3.16	21.1	-47	-56	≤ -70	≤ -70	-63	37.82	36.21
4	7	121.4	3.17	21.7	-55	-55	≤ -70	≤ -70	-61	38.43	36.92

Table 4: SX1262 Tx Characteristics as a Function of PaConfig (869.525 MHz; +22 dBm – Switchless)

Configuration (4; 7) indicates the condition for both maximum output power and efficiency, consistent with the default configuration noted in the SX1261/2 datasheet.

Finally, consider operating within ITU region 2, with a LoRaWAN uplink channel operating at 902.3 MHz and an output power of nominally +22 dBm.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
2	7	98.5	3.15	20.3	-39	≤ -70	≤ -70	≤ -70	-64	-53	-65	-66	-57	34.53	32.96
3	7	111.2	3.16	21.0	-42	≤ -70	≤ -70	≤ -70	-62	-53	-63	-67	-56	35.83	34.31
4	6	116.7	3.16	21.1	-41	-69	≤ -70	≤ -70	-61	-53	-64	-68	-56	34.93	33.45
4	7	124.9	3.17	21.6	-39	-69	≤ -70	≤ -70	-61	-52	-64	-66	-56	36.51	35.07

Table 5: SX1262 Tx Characteristics as a Function of PaConfig (902.3 MHz; +22 dBm - Switchless)

Again, configuration PaConfig(4; 7) indicates the condition for both maximum output power and efficiency. In addition, good harmonic rejection of both H2 (non-restricted band emission) and H3 (restricted band spurious emission) is obtained.

Implementing the same PA configuration at both 914.9 MHz and 927.5 MHz yields similar results, enabling the same parameter configuration values for the 26 MHz of available spectrum, as shown in Table 8.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
2	7	98.8	3.15	20.2	-39	≤ -70	≤ -70	≤ -70	-63	-55	-64	-67	-56	33.34	31.82
3	7	111.6	3.16	20.9	-39	≤ -70	≤ -70	≤ -70	-62	-55	-63	-67	-56	34.89	33.41
4	7	125.6	3.17	21.5	-36	≤ -70	≤ -70	≤ -70	-61	-53	-64	-66	-55	35.48	34.08

Table 6: SX1262 Tx Characteristics as a Function of PaConfig (914.9 MHz; +22 dBm - Switchless)

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
2	7	99.4	3.15	20.1	-38	≤ -70	≤ -70	≤ -70	-62	-57	-65	-68	-56	32.68	31.20
3	7	112.2	3.16	20.8	-37	≤ -70	≤ -70	≤ -70	-61	-56	-64	-69	-56	33.91	32.47
4	7	125.3	3.17	21.5	-35	≤ -70	≤ -70	≤ -70	-61	-55	-66	-69	-56	35.92	33.93

Table 7: SX1262 Tx Characteristics as a Function of PaConfig (927.5 MHz; +22 dBm - Switchless)

Table 10 shows an application where, for a particular mode of operation, the SX1262 TX is implemented as a pre-driver for an external PA or Front-End Module (FEM) where an output power of nominally +13.5 to +14 dBm is required, to ensure the optimum operating conditions for this external device.

PaDC	hpMax	TXCf _g (dBm)	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
					PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
0	3	22	45.5	3.12	13.7	-37	≤ -70	≤ -70	≤ -70	≤ -70	-60	≤ -70	≤ -70	-63	16.51	15.61
3	2	22	48.9	3.12	13.9	-44	≤ -70	≤ -70	≤ -70	≤ -70	-61	-69	≤ -70	-66	16.09	15.21
1	3	21	52.2	2.78	14.0	-40	≤ -70	≤ -70	≤ -70	-67	-60	≤ -70	≤ -70	-63	17.31	14.58
4	2	21	53.5	2.78	13.6	-47	≤ -70	≤ -70	≤ -70	≤ -70	-61	≤ -70	≤ -70	-64	15.40	12.98
2	3	20	58.6	2.49	13.9	-39	≤ -70	≤ -70	≤ -70	-69	-63	≤ -70	≤ -70	-62	16.82	12.69

Table 8: SX1262 Tx Characteristics as a Function of Tx and PaConfig (914.9 MHz; +14 dBm - Switchless)

With **TxPower** configured to maximize VR_PA, **PaConfig** configurations PaConfig(0; 3) and PaConfig(3; 2) meet the design brief and are consistent with the settings obtained for operation in the 863 – 870 MHz band. However, we see that by configuring the **TxPower** setting in tandem with **PaConfig**, a degree of fine-tuning can also be achieved, enabling further trade-off of the SX1262 operating characteristics.

To demonstrate the versatility of the reference design, the SX1262 is replaced with SX1261, while the BOM remains unmodified. **TxPower** is configured to +14 dBm for maximum efficiency and as previously noted, **hpMax** is set to 0. Again, operation in both the European and North American frequency bands is required.

Operation at 868.3 MHz is considered first, as tabulated below in Table 9.

PaDC	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)						η_{PA} (%)	η_{SX} (%)
			PTx	H2	H3	H4	H5	H6		
1	17.4	1.36	10.4	-42	-66	≤ -70	≤ -70	≤ -70	45.80	18.88
2	19.9	1.37	11.5	-43	≤ -70	≤ -70	≤ -70	≤ -70	51.93	21.56
3	22.7	1.37	12.6	-44	-62	≤ -70	≤ -70	≤ -70	57.84	24.01
4	25.8	1.38	13.4	-47	-61	≤ -70	≤ -70	≤ -70	61.45	25.70
5	29.1	1.38	14.2	-52	-59	≤ -70	≤ -70	≤ -70	65.20	27.26
6	32.9	1.38	14.8	-59	-58	≤ -70	≤ -70	≤ -70	66.21	27.69
7	36.6	1.39	15.2	-50	-58	≤ -70	≤ -70	≤ -70	65.09	27.42

Table 9: SX1261 Tx Characteristics as a Function of PaConfig (868.3 MHz; +14 dBm - Switchless)

Table 10 indicates the configuration parameters for operation at 902.3 MHz:

PaDC	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
			PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
1	16.8	1.36	9.8	-40	≤ -70	≤ -70	≤ -70	≤ -70	-62	≤ -70	≤ -70	-62	41.80	17.23
2	19.2	1.37	11.0	-41	≤ -70	≤ -70	≤ -70	≤ -70	-63	≤ -70	≤ -70	-64	47.86	19.87
3	21.9	1.37	12.1	-43	≤ -70	≤ -70	≤ -70	≤ -70	-60	≤ -70	≤ -70	≤ -70	54.05	22.44
4	24.8	1.38	13.0	-45	≤ -70	≤ -70	≤ -70	≤ -70	-59	≤ -70	≤ -70	-63	58.30	24.38
5	28.1	1.38	13.8	-51	-64	≤ -70	≤ -70	-64	-63	≤ -70	≤ -70	≤ -70	61.86	25.87
6	31.7	1.38	14.5	-57	-63	≤ -70	≤ -70	≤ -70	-64	-64	≤ -70	≤ -70	63.84	26.69
7	35.1	1.39	15.0	-48	-64	≤ -70	≤ -70	≤ -70	-61	≤ -70	≤ -70	≤ -70	64.37	27.11

Table 10: SX1261 Tx Characteristics as a Function of PaConfig (902.3 MHz; +14 dBm - Switchless)

Similarly, it can be demonstrated that the same PA configuration at both 914.9 MHz and 927.5 MHz yields similar results, again enabling the same parameter configurations to be used, as tabulated below in Table 11 and Table 12:

PaDC	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
			PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
5	27.9	1.38	13.7	-51	≤ -70	≤ -70	≤ -70	-64	≤ -70	≤ -70	≤ -70	-63	60.61	25.34
6	31.6	1.38	14.3	-54	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	-62	61.72	25.81

Table 11: SX1261 Tx Characteristics as a Function of PaConfig (914.9 MHz; +14 dBm - Switchless)

PaDC	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
			PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
5	27.9	1.38	13.7	-51	≤ -70	≤ -70	≤ -70	-64	≤ -70	≤ -70	≤ -70	-63	60.61	25.34
6	31.6	1.38	14.3	-54	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	-62	61.72	25.81

Table 12: SX1261 Tx Characteristics as a Function of PaConfig (927.5 MHz; +14 dBm - Switchless)

8.3 BOM: T/R Switch Reference Design

The SX1262 BOM TX and RX matching networks is shown below (basically designed for 915 MHz - North America):

RefDes	Package	Value	Qty	Description	Manufacturer
C1	0402	47nF	1	Multilayer ceramic capacitors X7R $\pm 10\%$, 16V	Murata
C2	0402	47pF	1	Multilayer ceramic capacitors C0G $\pm 5\%$, 50V	Murata
C3	0402	NC	0	Not Populated	Murata
C4	0402	3.0pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C5	0402	5.6pF	1	Multilayer ceramic capacitors C0G $\pm 0.25\text{pF}$, 50V	Murata
C6	0402	39pF	1	Multilayer ceramic capacitors C0G $\pm 5\%$, 50V	Murata
C7	0402	1.8pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C8	0402	39pF	1	Multilayer ceramic capacitors C0G $\pm 5\%$, 50V	Murata
C9	0402	3.3pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C10	0402	3.3pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C11	0402	2.4pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
C12	0402	1.8pF	1	Multilayer ceramic capacitors C0G $\pm 0.1\text{pF}$, 50V	Murata
L1	0402	47nH	1	Wirewound Inductor $\pm 5\%$	Murata
L2	0402	0R	1	Thick Film Resistor $\pm 1\%$, 1/16W	Vishay/Dale
L3	0402	2.5nH	1	Wirewound Inductor $\pm 0.2\text{nH}$	Murata
L4	0402	4.7nH	1	Wirewound Inductor $\pm 0.2\text{nH}$	Murata
L5	0402	9.1nH	1	Wirewound Inductor $\pm 3\%$	Murata
L6	0402	15nH	1	Wirewound Inductor $\pm 3\%$	Murata

Table 13: SX1262 T/R Switch Reference Design (E428V03A) - BOM

8.4 Adaptive Matching Configuration

As with the switchless design, configurations for three typical application scenarios will be demonstrated:

1. Operation as a default LoRaWAN channel operating at 868.3 MHz with an approximate ERP of 25 mW (+14 dBm)
2. Operation as a LoRaWAN channel operating in at 869.525 MHz with an approximate ERP of 158 mW (+22 dBm)
3. Operation as a LoRaWAN channel operating at 902.3 MHz with an approximate output power of +22 dBm

We consider the case for operation at 868.3 MHz with a nominal output power of +14 dBm (± 1 dB) as documented below in Table 14.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)						η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6		
0	3	46.7	3.11	13.8	-39	-51	≤ -70	≤ -70	≤ -70	16.33	15.39
2	2	44.3	3.11	13.3	-41	-61	≤ -70	≤ -70	≤ -70	15.45	14.56
3	2	49.1	3.11	14.1	-41	-54	≤ -70	≤ -70	≤ -70	16.91	15.94

Table 14: SX1262 Tx Characteristics as a Function of PaConfig (868.3 MHz; +14 dBm - Switched)

From the results shown in Table 16, it can again be noted that PaConfig parameters (0; 3), (2; 2), (3; 2) result in the required indicated fundamental output power. Configuration PaConfig(2; 2) provides for the lowest current consumption and good harmonic balance, while configuration PaConfig(3; 2) indicates the conditions for maximum efficiency.

In the second application scenario, operation at 869.525 MHz with a nominal output power of +22 dBm is tabulated below in Table 15.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)						η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6		
3	7	116.4	3.16	21.6	-36	-44	≤ -70	≤ -70	≤ -70	39.30	37.63
4	7	127.0	3.16	22.1	-38	-43	≤ -70	≤ -70	≤ -70	40.79	39.06

Table 15: SX1262 Tx Characteristics as a Function of PaConfig (869.525 MHz; +22 dBm - Switched)

Again, configuration PaConfig(4; 7) indicates the condition for both maximum output power and efficiency, consistent with the default configuration noted in the datasheet.

If operation at +14 dBm is required, the configurations highlighted previously in Table 14 apply:

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)						η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6		
0	3	46.6	3.11	13.9	-39	-51	≤ -70	≤ -70	≤ -70	16.74	15.78
2	2	44.3	3.10	13.3	-41	-60	≤ -70	≤ -70	≤ -70	15.57	14.62
3	2	49.1	3.11	14.1	-42	-54	≤ -70	≤ -70	≤ -70	16.99	16.01

Table 16: SX1262 Tx Characteristics as a Function of PaConfig (869.525 MHz; +14 dBm - Switched)

Finally, we consider operation within ITU region 2, and consider a LoRaWAN uplink channel operating at 914.9 MHz with an output power of nominally +22 dBm.

PaDC	hpMax	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
3	7	110.1	3.16	21.4	-49	-54	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	39.68	37.99
4	7	118.2	3.15	21.8	-49	-52	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	40.65	38.80

Table 17: SX1262 Tx Characteristics as a Function of PaConfig (902.3 MHz; +22 dBm - Switched)

As gain, configuration PaConfig(4; 7) indicates the condition for both maximum output power and efficiency, and can be applied to any LoRaWAN channel configured for operation in the 902 – 928 MHz band.

Similarly, the SX1262 can also be replaced by SX1261, like in the SX1262MB1PAS reference design PCB_E449V01A [5], with DC-DC configuration and mode used (L8 = 47nH and R18 = NC for SX1261), while the published RF BOM remains unmodified. IDDTx current measurements doesn't include the TCXO consumption in table 19:

RefDes	Package	Value	Qty	Description	Manufacturer
U1	SX1261IMLRT	VQFN24 4x4mm	1	150MHz to 960MHz Low Power Long Range Transceiver	Semtech
R18	0402	NC	0	Not Populated	Murata
L8	0402	47nH	1	Wirewound Inductor $\pm 5\%$	Murata

Table 18: SX1261 BOM changes for DC-DC mode configuration from SX1262MB1PAS Reference Design (E449V01A) - BOM

Freq. (MHz)	PaDC	IDDTx (mA)	VR_PA (V)	TX Output Power (dBm)										η_{PA} (%)	η_{SX} (%)
				PTx	H2	H3	H4	H5	H6	H7	H8	H9	H10		
868.3	4	25.1	1.38	12.9	-46	-62	≤ -70	≤ -70	≤ -70					56.29	23.54
902.3	6	31.4	1.38	13.8	-55	-65	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	55.36	23.15
914.9	6	30.8	1.38	13.7	-53	-67	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	55.15	23.06
927.5	6	30.7	1.38	13.5	-52	-67	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	≤ -70	52.84	22.10

Table 19: SX1261 Tx Characteristics as a Function of PaConfig and Frequency (+14 dBm - Switched)

8.5 Design Considerations

As documented in this Application Note the transmitter matching network is a cascaded low-pass filter topology with the addition of a harmonic trap formed by C6, L2 (Switchless design) or C4, L3 (Switched design). The harmonic trap is required to attenuate the H2 component while operating in Europe and H3 in North America.

As such “fine-tuning” of the network may be required in terms of both hardware BOM and FW configurations depending upon the PCB layout, Layers stack-up definition and substrate, layers separation and both component series and tolerance.

9 Receiver Adaptive Match Design Methodology

As described in Section 5, a PER (Packets Error Rate) measurement is performed at the frequencies of interest for each possible configuration of **lna_cap_tune_n** and **lna_cap_tune_p** in turn.

The receiver under test is placed in a shielded RF enclosure and the PER, as a function of **lna_cap_tune**, is measured with a suitably modulated signal conducted at the antenna port.

A 10% PER metric is used as an indication of the receiver sensitivity, since this provides for a more repeatable threshold level than 1% PER. The minimum number of packets transmitted for each measurement is 1000 to ensure that a minimum of 100 packets received in error (10% of the total transmitted) can be used as an indication of the sensitivity level.

Note that this process will reveal a range of values of **lna_cap_tune_n** and **lna_cap_tune_p** over which an optimized sensitivity level is indicated, subject to the granularity provided by the PER measurement. It is recommended that the identified range be verified on several devices to ensure the component tolerances of the external matching network are taken into consideration.

In the examples below, we consider an application intended to operate over both European and North American ISM bands over a frequency range from 863 - 928 MHz with a single hardware BOM. For each possible configuration of **lna_cap_tune** the resultant PER was validated with a 64 bytes packet at CR = 4/5 with payload CRC enabled at BW = 125 kHz, SF = 7.

9.1 SX1261/2 Switchless Reference Design (E460V01A)

As illustrated in Figure 13, the transmitter and receiver networks of the switchless reference design are part of the same matching network. With the transmit circuit previously optimized, optimization of receiver performance can be purely implemented through firmware configuration as summarized below in Table 20.

lna_cap_tune		10% PER Sensitivity Threshold (dBm) at Test Frequency (MHz)				
n	p	863.3	869.525	902.3	914.9	927.5
0x4	0x4	-125	-125	-125	-125	-126
0x0	0x0	-125	-125	-125	-125	-126
0x0	0x8	-125	-125	-125	-125	-126
0x0	0xF	-125	-125	-125	-125	-126
0x4	0x0	-125	-125	-125	-125	-126
0x4	0x8	-125	-125	-126	-126	-126
0x4	0xF	-125	-126	-126	-126	-126
0x8	0x0	-125	-125	-125	-125	-126
0x8	0x8	-125	-126	-126	-126	-126
0x8	0xB	-125	-126	-126	-126	-126
0x8	0xF	-126	-126	-126	-126	-126
0xB	0x0	-125	-126	-126	-126	-126
0xB	0x8	-125	-126	-126	-126	-126
0xB	0xB	-125	-126	-126	-126	-126
0xB	0xF	-125	-126	-126	-126	-126
0xF	0x0	-125	-125	-125	-125	-126
0xF	0x8	-126	-126	-126	-126	-126
0xF	0xF	-126	-126	-126	-126	-126

Table 20: 10% PER Threshold as a Function of lna_cap_tune (Switchless Design)

From the results obtained, it can be observed that for value pairs of **lna_cap_tune_n** 0xF and **lna_cap_tune_p** 0x8 - 0xF, a 10% PER sensitivity threshold of at least -126 dBm is obtained over the entire frequency band of interest.

It should be noted that by comparing the indicated PER value for at the sensitivity threshold over the range of possible **lna_cap_tune** combinations, the indicated sensitivity degradation is less than < 1 dB.

Due to the Q-factor associated with the matching network and the associated component tolerances it is recommend that if firmware configuration is implemented that values of **lna_cap_tune** are selected from a mid-position over a contiguous range of values that provide the required sensitivity level.

9.2 SX1262 T/R Switch Reference Design (E428V03A)

As illustrated in Figure 15, the transmitter and receiver networks of the SX1262MB1CAS mbed shield reference design are isolated by the T/R switch and thus either the receiver hardware matching network or the port configuration can be optimized independently of the transmitter circuit, as summarized below in Table 21.

lna_cap_tune		10% PER Sensitivity Threshold (dBm) at Test Frequency (MHz)				
n	p	863.3	869.525	902.3	914.9	927.5
0x4	0x4	-126	-126	-126	-126	-126
0x0	0x0	-126	-126	-126	-126	-126
0x0	0x8	-126	-126	-126	-126	-126
0x0	0xF	-126	-126	-126	-126	-126
0x4	0x0	-126	-126	-126	-126	-126
0x4	0x8	-126	-126	-126	-126	-126
0x4	0xF	-126	-126	-126	-126	-126
0x8	0x0	-126	-126	-126	-125	-126
0x8	0x8	-126	-126	-125	-125	-125
0x8	0xF	-126	-126	-125	-125	-125
0xB	0x0	-126	-126	-125	-125	-125
0xB	0x8	-126	-126	-125	-125	-125
0xB	0xF	-126	-126	-125	-125	-125
0xF	0x0	-126	-126	-125	-125	-125
0xF	0x8	-126	-126	-125	-125	-125
0xF	0xF	-126	-126	-125	-125	-125

Table 21: 10% PER Threshold as a Function of lna_cap_tune (T/R Switch Design)

From the results obtained it can be observed that for value pairs of **lna_cap_tune_n** from 0x0 to 0x04 and **lna_cap_tune_p** from 0x0 to 0xF, a 10% sensitivity threshold of at least -126 dBm is obtained over the entire frequency band of interest. It should be noted that the indicated sensitivity in the European ISM band is insensitive to the values of **lna_cap_tune** configured.

Above these configured values (i.e. port loading capacitance increases), there is a small degradation in indicated PER, although it should be noted that by comparing the indicated PER value for at the sensitivity threshold, the degradation is less than < 1 dB when the indicated PER value at the sensitivity threshold is taken into consideration.

10 Conclusions

This Application Note demonstrates that both the transmitter PA and receiver input capacitance configuration of both SX1261 and SX1262 can be manipulated by firmware to provide additional tools to assist the RF design process.

The Application Note also describes a lower-cost reference design that does not require a T/R switch, which can be utilized for both SX1261 and SX1262 designs. It describes a methodology for designing a common hardware BOM covering the frequency range and differing transmit output power requirements of the 863 to 928 MHz using the adaptive matching techniques described.

Finally, this Application Note demonstrates that these techniques can be applied to existing circuit designs that incorporate a switch between antenna and the transmitter and receiver ports.

11 References

[1] SX1261/SX1262 Datasheet

[SX1261/SX1262 Datasheet](#)

[2] SX1261MB1LDCS & SX1262MB1LDCS mbed Shields – Reference Design only

<https://www.semtech.com/products/wireless-rf/lora-connect/sx1261mb1ldcs>

<https://www.semtech.com/products/wireless-rf/lora-connect/sx1262mb1ldcs>

[3] SX1262MB2CAS mbed shield - included in SX1262DVK1CAS Development Kit

<https://www.semtech.com/products/wireless-rf/lora-connect/sx1262dvk1cas>

[4] ERC Recommendation 70-03

<https://docdb.cept.org/download/25c41779-cd6e/Rec7003e.pdf>

[5] SX1262MB1PAS mbed shield - included in SX1262DVK1PAS Development Kit

<https://www.semtech.com/products/wireless-rf/lora-connect/sx1262dvk1pas>

12 Revision History

Version	ECO	Date	Changes and/or Modifications
1.0	056885	May 2021	Initial Version
1.1	070660	March 2024	Update of the template document and value for L1 inductor in BOM (typo)



Important Notice

Information relating to this product and the application or design described herein is believed to be reliable, however such information is provided as a guide only and Semtech assumes no liability for any errors in this document, or for the application or design described herein.

Semtech reserves the right to make changes to the product or this document at any time without notice. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. Semtech warrants performance of its products to the specifications applicable at the time of sale, and all sales are made in accordance with Semtech's standard terms and conditions of sale.

SEMTECH PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR IN NUCLEAR APPLICATIONS IN WHICH THE FAILURE COULD BE REASONABLY EXPECTED TO RESULT IN PERSONAL INJURY, LOSS OF LIFE OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. INCLUSION OF SEMTECH PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE UNDERTAKEN SOLELY AT THE CUSTOMER'S OWN RISK.

Should a customer purchase or use Semtech products for any such unauthorized application, the customer shall indemnify and hold Semtech and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs damages and attorney fees which could arise.

The Semtech name and logo are registered trademarks of the Semtech Corporation. All other trademarks and trade names mentioned may be marks and names of Semtech or their respective companies. Semtech reserves the right to make changes to, or discontinue any products described in this document without further notice. Semtech makes no warranty, representation or guarantee, express or implied, regarding the suitability of its products for any particular purpose. All rights reserved.

© Semtech 2024